

RC, RL, RCL FORMULAE & CIRCUITS

USAOMMCS X - 14319


Revised Jan 2002

TYPE OF CIRCUIT	TC/PW RATIO			
	100	10	1	100
RC, LR	100	10	1	100
EA EA	100	10	1	100
ER EL	100	10	1	100
EC ER	100	10	1	100


TC/PW Ratio
SHORT: EQUAL TO OR LESS THAN 1/10
MEDIUM: FROM 1/10 TO 10/1 (NOT USED)
LONG: EQUAL TO OR GREATER THAN 10/1

$$TC = RC \quad TC = \frac{L}{R} \quad PW = \frac{1}{2f} \quad \text{For a symmetrical square wave}$$


DIFFERENTIATOR A CIRCUIT THAT CHANGES A SQUARE WAVE INTO A PEAKED WAVE.
 INTEGRATOR A CIRCUIT THAT CHANGES A PEAKED WAVE INTO A TRIANGLE WAVE.
 COUPLER OUTPUT WAVE FORM IS IDENTICAL TO INPUT WAVE FORM.
 PULSE WIDTH THE DURATION OF A PULSE EXPRESSED IN TIME. THE TIME BETWEEN THE LEADING EDGE AND THE TRAILING EDGE
 TRANSIENT A TRANSIENT IS A CHANGING VOLTAGE OR CURRENT FROM ONE STEADY STATE TO ANOTHER. THE TERM TRANSIENT HAS BEEN EXPANDED TO INCLUDE ANY NONSINUSOIDAL VOLTAGE.

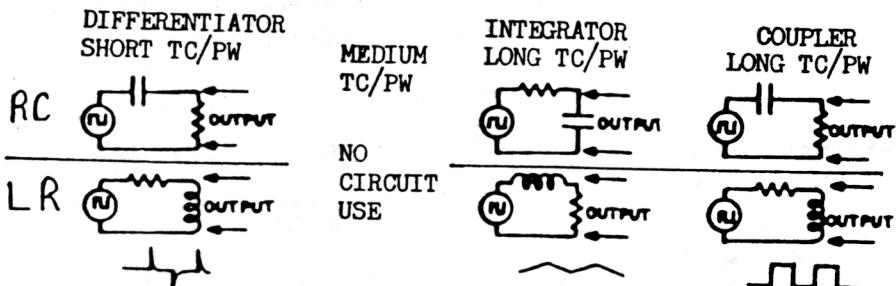

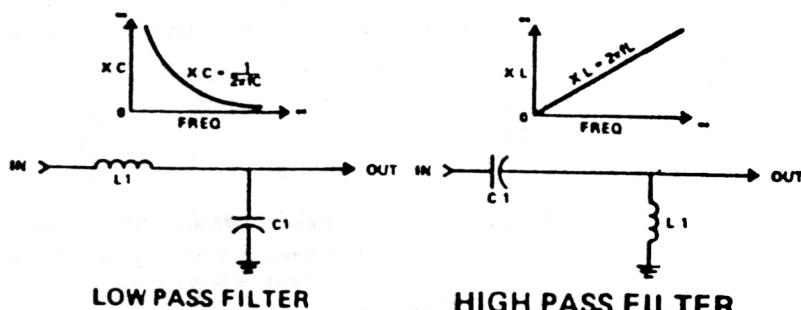COUPLER CIRCUIT OUTPUT WAVE SHAPE IS IDENTICAL TO THE INPUT WAVE SHAPE THEREFORE THE TC IS VERY LONG.



UNIVERSAL TIME CONSTANT CHART

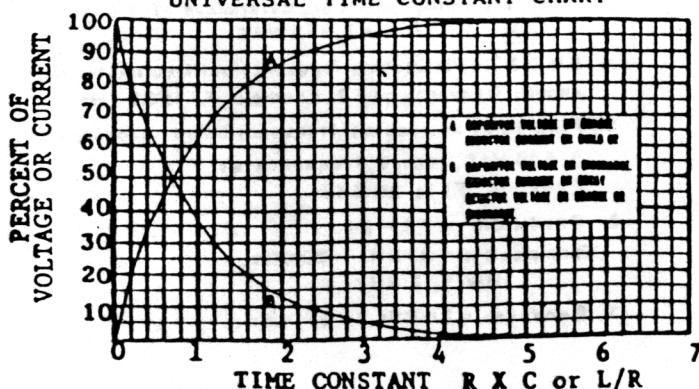

PERCENT VOLTAGE


TC	Chg	Disch
1	63.2	36.8
2	86.5	13.5
3	95	5.0
4	98	2.0
5	99	1.0

RC, RL, RCL FORMULAE & CIRCUITS


USAOMMCS X-14319

Revised Jan 2002

SERIES RESONANCE BAND

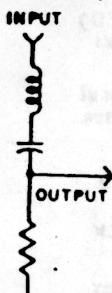


PASS FILTER

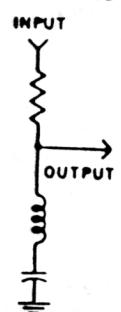


REJECT FILTER

PARALLEL RESONANCE BAND

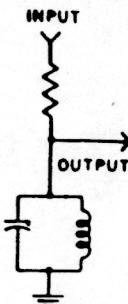

PASS FILTER

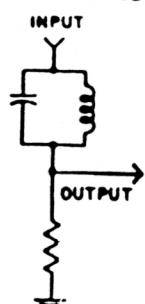

REJECT FILTER

	BELOW f_r CAPACITIVE	AT f_r RESISTIVE	ABOVE f_r INDUCTIVE	VOLTAGE/CURRENT RELATIONSHIP
SERIES	$X_c > X_L$ $E_c > E_L$	$X_c = X_L$ $E_c = E_L$	$X_L > X_c$ $E_L > E_c$	
	I decrease Z increase	I maximum	I decrease Z increase	
PARALLEL	$X_c > X_L$ $I_L > I_c$	$X_c = X_L$ $I_c = I_L$	$X_L > X_c$ $I_c > I_L$	
	I increase Z decrease	I minimum Z maximum	I increase Z decrease	
	INDUCTIVE	RESISTIVE	CAPACITIVE	

BANDWIDTH-QUALITY BAND PASS CIRCUITS

P_k
TOTAL X

$BW = f_2 - f_1$

$Q = \frac{f_r}{BW} = \frac{X_L}{R} = \frac{X_C}{R}$

HI Q f_1 f_2 Low Q f_1 f_2

RESONANCE

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{159}{\sqrt{LC}}$$


$$X_L = 2\pi f L$$

$$X_C = \frac{1}{2\pi f C}$$



$$I = \frac{E_c}{X_C}$$

$$I = \frac{E_A}{Z}$$
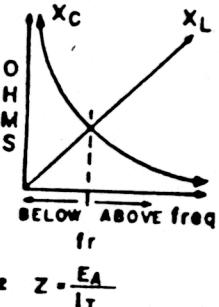
$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad Z = \frac{E_A}{I_T}$$



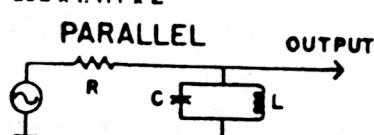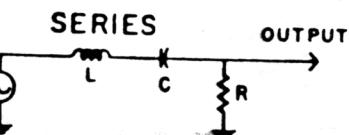EFFECTIVE VALUE = PEAK TO PEAK VALUE $\times 0.707 \div 2$
PEAK TO PEAK VALUE = EFFECTIVE VALUE $\times 1.414 \times 2$



EXAMPLE OF DETERMINING BANDWIDTH USING TEST EQUIPMENT

- Find Resonance Frequency by varying the input frequency so that the output voltage (circuits above) is maximum.
- Record Resonance Frequency and the voltage at resonant. Example: Assume a maximum voltage of 5 VAC at a frequency of 25 KHz.
- Bandpass voltage points are determined at .707 of maximum voltage. Example: $5 \times .707 = 3.535$ VAC
- Find F2 by increasing frequency until voltmeter reads 3.535 VAC, record frequency as F2. Example: F2 is 33 KHz
- Find F1 by decreasing frequency below resonance until voltmeter reads 3.535 VAC, record frequency as F1. Example: F1 is 20 KHz
- Bandwidth = F2 - F1.
Example: BW = 33 KHz - 20 KHz,
BW = 13 KHz
- Bandpass = 20 KHz to 33 KHz